

Data Hazards:

Type: Compute-use hazard Reason:

Data computed after the execute stage is not written until the write back step is complete. During the Decode stage, a succeeding instruction could read the incorrect data from the previous instruction's destination register. The source register for the following instruction has not yet been updated with the right data value.

Affected Stages:

Following the instruction is the decode stage, where the computation will provide the incorrect data value. As a result, the Execute and WriteBack stages will execute actions using incorrect data values.

When It Occurs:

When the R type instruction add is being executed, an example can be shown. When the source registers for the following instruction (rs) or the target register (rt) request access to the destination register (rd) of the preceding instruction, the destination register (rd) of the R-type instruction is not yet written.

Type: Load-use hazard Reason:

Until the Memory stage is complete, instructions that require reading from memory cannot read data values. Thus, a future instruction cannot access data that was loaded from memory during a prior instruction's execution during the Execute stage.

Affected Stages:

This two-cycle latency may have an impact on the Execute and Memory stages (in the event that memory writes).

When It Occurs:

A hazard occurs when a subsequent instruction attempts to access data in memory that was loaded by a previous instruction.

Type: Load-store hazard Reason:

When data wanted to store at a memory location just after immediately loaded from memory.

Affected Stages:

Memory stage of storing instruction will be affected because wrong data will be stored in memory location.

When It Occurs:

Consecutive lw and sw instructions are being used with same rt register. **Control Hazards:**

Type: Branch hazard

Reason:

Branch decision is not made by the time next instruction is fetched from the instruction memory. The branch prediction is made at Memory stage which causes delay.

Affected Stages:

Due to delay at branch prediction unnecessary 3 instructions will be fetched in the case of branch misprediction.

When It Occurs: When a branch decision is needed.

Solutions:

Solution for Compute Use hazard:

When the R-type instruction add is being executed, an example can be shown. When the source registers for the following instruction (rs) or the target register (rt) request access to the destination register (rd) of the preceding instruction, the destination register (rd) of the R-type instruction is not yet written.

Solution for Load Use Hazard:

Forwarding does not solve this problem. A pause is a type of solution where the pipeline is held until data is available.

Solution for Load Store Hazard:

Stalling is an effective strategy to allow loading from memory done until subsequent instruction fetches data from same register at its Decode stage.

Solution for Branch Hazard:

Pipeline can be stalled for 3 cycles or with additional hardware (equality comparators) branch decision can be made at an earlier stage. Flushing the fetched instructions is also important to fix branch mispredictions.

Logic of Hazard Unit for Forwarding

if ((rsE != 0) AND (rsE == WriteRegM) AND RegWriteM) then ForwardAE = 10

else if ((rsE != 0) AND (rsE == WriteRegW) AND RegWriteW) then ForwardAE = 01

else ForwardAE = 00

Logic of Hazard Unit for Stalling & Flushing

lwstall = ((rsD == rtE) OR (rtD == rtE)) AND MemtoRegE StallF = StallD = FlushE = lwstall

No hazards

addi \$t0,
addi \$t1,
addi \$t2,
or \$t3, \$t1, \$t2 add \$t4, \$t0, \$t1 sub \$t5, \$t2, \$t0 sw \$t0, 10(\$t4) lw \$t5,
8(\$zero) beq \$t1, \$zero, 1 sub \$t1, \$t1, \$t2 and \$t4, \$t2, \$t3

Compute Use Hazard

addi \$t0, \$zero, 8 addi \$t1, \$zero, 9 sub \$t2, \$t1, \$t0 **Load Use Hazard** addi
\$t0, \$zero, 5 addi \$t1, \$zero, 10 addi \$t2, \$zero, 15 lw \$t0, 10(\$t1) add \$t3,
\$t0, \$t2 sub \$t4, \$t2, \$t0

Load Store hazard

addi \$t0, \$zero, 8 addi \$t1, \$zero, 7 addi \$t2, \$zero, 6

\$zero, 1

\$zero, 2

\$zero, 3

lw \$t0, 6(\$t1)

sw \$t0, 7(\$t3)

Branch Hazard

addi \$t0, \$zero, 4 addi \$t1, \$zero, 4 addi \$t2, \$zero, 3 addi \$t3, \$zero, 5 beq
\$t0, \$t1, Continue

addi \$t5, \$zero, 9

add \$t0, \$t1, \$t2 or \$t3, \$t2, \$t1 addi \$t6, \$zero, 7 Continue:
and \$t0, \$t0, \$t1

System Verilog Code

timescale 1ns / 1ps

// Define pipes that exist in the PipelinedDatapath.
// The pipes between Writeback (W) and Fetch (F), as well as Decode (D) and Execute (E)
are given to you.
// Create the rest of the pipes where inputs follow the naming conventions in the book.

```
module PipeFtoD(input logic[31:0] instrF, PcPlus4F,  
               input logic EN, clear, clk, reset,  
               output logic[31:0] instrD, PcPlus4D);  
  
    always_ff @(posedge clk, posedge reset)  
        if(reset)  
            begin  
                instrD <= 0;  
                PcPlus4D <= 0;  
            end  
        else if(EN)  
            begin  
                if(clear)  
                    begin  
                        instrD <= 0;  
                        PcPlus4D <= 0;  
                    end  
                else  
                    begin  
                        instrD <= instrF;  
                        PcPlus4D <= PcPlus4F;  
                    end  
            end  
    end  
  
endmodule
```

// The pipe between Writeback (W) and Fetch (F) is given as follows.

```
module PipeWtoF(input logic[31:0] PC,  
               input logic EN, clk, reset,           // ~StallF will be connected as this EN  
               output logic[31:0] PCF);  
  
    always_ff @(posedge clk, posedge reset)  
        if(reset)  
            PCF <= 0;  
        else if(EN)  
            PCF <= PC;  
    endmodule
```

```

module PipeDtoE(input logic[31:0] RD1, RD2, SignImmD,
    input logic[4:0] RsD, RtD, RdD,
    input logic RegWriteD, MemtoRegD, MemWriteD, ALUSrcD,
    input logic [1:0] RegDstD,
    input logic[2:0] ALUControlD,
    input logic clear, clk, reset, EN,
    output logic[31:0] RsData, RtData, SignImmE,
    output logic[4:0] RsE, RtE, RdE,
    output logic RegWriteE, MemtoRegE, MemWriteE, ALUSrcE,
    output logic [1:0] RegDstE,
    output logic[2:0] ALUControlE);

```

```

always_ff @(posedge clk, posedge reset)

```

```

    if(reset || clear)

```

```

        begin

```

```

            // Control signals

```

```

            RegWriteE <= 0;

```

```

            MemtoRegE <= 0;

```

```

            MemWriteE <= 0;

```

```

            ALUControlE <= 0;

```

```

            ALUSrcE <= 0;

```

```

            RegDstE <= 0;

```

```

            // Data

```

```

            RsData <= 0;

```

```

            RtData <= 0;

```

```

            RsE <= 0;

```

```

            RtE <= 0;

```

```

            RdE <= 0;

```

```

            SignImmE <= 0;

```

```

        end

```

```

    else if (EN)

```

```

        begin

```

```

            // Control signals

```

```

            RegWriteE <= RegWriteD;

```

```

            MemtoRegE <= MemtoRegD;

```

```

            MemWriteE <= MemWriteD;

```

```

            ALUControlE <= ALUControlD;

```

```

            ALUSrcE <= ALUSrcD;

```

```

            RegDstE <= RegDstD;

```

```

            // Data

```

```

            RsData <= RD1;

```

```

            RtData <= RD2;

```

```

            RsE <= RsD;

```

```

            RtE <= RtD;

```

```

    RdE <= RdD;
    SignImmE <= SignImmD;
end

```

```
endmodule
```

```

module PipeEtoM(input logic clk, reset, EN, RegWriteE, MemtoRegE, MemWriteE,
    input logic [31:0] ALUOutE, WriteDataE,
    input logic [4:0] WriteRegE,
    output logic RegWriteM, MemtoRegM, MemWriteM, output logic [31:0] ALUOutM,
    WriteDataM, output logic [4:0] WriteRegM);

```

```

    always_ff @(posedge clk, posedge reset)
        if(reset)
            begin
                // Control signals
                RegWriteM <= 0;
                MemtoRegM <= 0;
                MemWriteM <= 0;

                // Data
                ALUOutM <= 0;
                WriteDataM <= 0;
                WriteRegM <= 0;
            end

        else if (EN)
            begin
                // Control signals
                RegWriteM <= RegWriteE;
                MemtoRegM <= MemtoRegE;
                MemWriteM <= MemWriteE;

                // Data
                ALUOutM <= ALUOutE;
                WriteDataM <= WriteDataE;
                WriteRegM <= WriteRegE;
            end

```

```
endmodule
```

```

module PipeMtoW (input logic clk, reset, EN, RegWriteM, MemtoRegM,
    input logic [31:0] ReadDataM, ALUOutM,
    input logic [4:0] WriteRegM,
    output logic RegWriteW, MemtoRegW,
    output logic [31:0] ReadDataW, ALUOutW,
    output logic [4:0] WriteRegW);

```

```

always_ff @(posedge clk, posedge reset)
    if(reset)
        begin
            // Control signals
            RegWriteW <= 0;
            MemtoRegW <= 0;

            // Data
            ALUOutW <= 0;
            ReadDataW <= 0;
            WriteRegW <= 0;
        end

    else if (EN)
        begin
            // Control signals
            RegWriteW <= RegWriteM;
            MemtoRegW <= MemtoRegM;

            // Data
            ALUOutW <= ALUOutM;
            ReadDataW <= ReadDataM;
            WriteRegW <= WriteRegM;
        end
endmodule

// *****
// End of the individual pipe definitions.
// *****

// *****
// Below is the definition of the datapath.
// The signature of the module is given. The datapath will include (not limited to) the following
// items:
// (1) Adder that adds 4 to PC
// (2) Shifter that shifts SignImmD to left by 2
// (3) Sign extender and Register file
// (4) PipeFtoD
// (5) PipeDtoE and ALU
// (5) Adder for PcBranchD
// (6) PipeEtoM and Data Memory
// (7) PipeMtoW
// (8) Many muxes
// (9) Hazard unit
// ...?
// *****

```

```

module datapath (input logic clk, reset,
    input logic[2:0] ALUControlD,
    input logic RegWriteD, MemtoRegD, MemWriteD, ALUSrcD,
    input logic [1:0] RegDstD,
    input logic BranchD,
    input logic jal,
    output logic [31:0] instrF,
    output logic [31:0] instrD, PC, PCF,
    output logic PcSrcD,
    output logic [31:0] ALUOutE, WriteDataE,
    output logic [1:0] ForwardAE, ForwardBE,
    output logic ForwardAD, ForwardBD,
    output logic [31:0] jalAdressD, output logic StallJal, FlushE); // Add or remove
input-outputs if necessary

```

```

// *****
// Here, define the wires that are needed inside this pipelined datapath module
// *****

```

```

/* We have defined a few wires for you
logic [31:0] PcSrcA, PcSrcB, PcBranchD, PcPlus4F;
logic [31:0] SignImmD, ShiftedImmD;
logic [31:0] ResultW;
logic [4:0] WriteRegW;
logic [31:0] RD1, RD2;
logic [31:0] SrcBE;
logic [31:0] ReadDataM;

logic [31:0] ReadDataW;
logic [31:0] ALUOutW;

```

```

    logic StallF;
    // logic FlushE;
    logic StallD;
logic RegWriteW;
logic [4:0] WriteRegE;
logic RegWriteM;
logic MemtoRegM;
logic [4:0] WriteRegM;
logic RegWriteE;
logic MemtoRegE;
logic MemWriteE;
logic ALUSrcE;
logic[1:0] RegDstE;
logic MemWriteM;
logic MemtoRegW;
logic EqualD;

```



```
logic [4:0] rsE;
logic [4:0] rtE;
logic [4:0] rdE;
logic [4:0] rsD;
logic [4:0] rtD;
logic [4:0] rdD;
```

```
logic [31:0] PcPlus4D;
logic [31:0] RsData;
logic [31:0] RtData;
logic [31:0] SignImmE;
logic [31:0] ALUOutM;
logic [31:0] WriteDataM;
logic [2:0] ALUControlE;
logic [31:0] rtMuxOut;
logic [31:0] rdMuxOut;
logic [31:0] SrcAE;
logic [31:0] newResult;
logic zero;
// logic StallJal;
```

/* You should define others down below (you might want to rename some of the wires above while implementing the pipeline)

/* We have provided you with a single-cycle datapath

/* You should convert it to a pipelined datapath, changing the connections between modules as necessary

```
// Replace with PipeWtoF
// flopr #(32) pcreg(clk, reset, PC, PCF);
PipeWtoF pipewf(PC, ~StallF, clk, reset, PCF);

// Do some operations
assign PcPlus4F = PCF + 4;
assign PcSrcB = PcBranchD;
    assign PcSrcA = PcPlus4F;
    logic [31:0] PCtemp;
    mux2 #(32) pc_mux(PcSrcA, PcSrcB, PcSrcD, PCtemp);
    assign jalAdressD = {PcPlus4D[31:28], instrD[25:0], 2'b00};
    mux2 #(32) jal_mux(PCtemp, jalAdressD, jal, PC);
    imem im1(PCF[7:2], instrF);
```

/* Replace the code below with

```
// assign instrD = instrF;
PipeFtoD pipefd(instrF, PcPlus4F,
    ~StallD, (PcSrcD || jal), clk, reset,
    instrD, PcPlus4D);
```

```

mux2 #(32) wrMux(ResultW, PcPlus4D, jal, newResult);
    // Decode stage
    regfile rf(clk, reset, RegWriteW, instrD[25:21], instrD[20:16], WriteRegW, newResult,
RD1, RD2);
    signext se(instrD[15:0], SignImmD);

    sl2 shiftimm(SignImmD, ShiftedImmD);
    adder branchadd(PcPlus4D, ShiftedImmD, PcBranchD);
    assign rsD = instrD[25:21];
    assign rtD = instrD[20:16];
    assign rdD = instrD[15:11];

mux2 #(32) rdMux(RD1,ALUOutM,ForwardAD,rdMuxOut);
mux2 #(32) rtMux(RD2,ALUOutM,ForwardBD,rtMuxOut);

assign EqualD = (rdMuxOut == rtMuxOut) ? 1 : 0;

assign PcSrcD = (EqualD && BranchD);

// Instantiate PipeDtoE here
PipeDtoE pipede(RD1, RD2, SignImmD,
    rsD, rtD, rdD,
    RegWriteD, MemtoRegD, MemWriteD, ALUSrcD, RegDstD,
    ALUControlD,
    FlushE, clk, reset, ~StallJal,
    RsData, RtData, SignImmE,
    rsE, rtE,rdE,
    RegWriteE, MemtoRegE, MemWriteE, ALUSrcE, RegDstE,
    ALUControlE);

// Execute stage
mux4 #(32) fourmux1(RtData, ResultW, ALUOutM, 32'bx, ForwardBE, WriteDataE);
    mux2 #(32) srcBMux(WriteDataE,SignImmE,ALUSrcE,SrcBE);

mux4 #(32) fourmux2(RsData,ResultW,ALUOutM,32'bx,ForwardAE,SrcAE);
    //mux2 #(5) wrMux(rtE, rdE, RegDstE, WriteRegE);
    mux4 #(5) wr4Mux(rtE, rdE,5'b11111,5'bx, RegDstE, WriteRegE);

alu alu(SrcAE, SrcBE, ALUControlE, ALUOutE, zero);

// Replace the code below with PipeEtoM
// assign WriteDataE = RD2;
PipeEtoM pipeem(clk, reset, ~StallJal, RegWriteE, MemtoRegE, MemWriteE,
    ALUOutE, WriteDataE,
    WriteRegE,
    RegWriteM, MemtoRegM, MemWriteM,
    ALUOutM, WriteDataM,
    WriteRegM);

```

```

// Memory stage
dmem DM(clk, MemWriteM, ALUOutM, WriteDataM, ReadDataM);

// Instantiate PipeMtoW
PipeMtoW pipemw(clk, reset, ~StallJal, RegWriteM, MemtoRegM,
    ReadDataM, ALUOutM,
    WriteRegM,
    RegWriteW, MemtoRegW,
    ReadDataW, ALUOutW,
    WriteRegW);

// Writeback stage
mux2 #(32) wbmux(ALUOutW, ReadDataW, MemtoRegW, ResultW);

HazardUnit hazardUnit(RegWriteW, BranchD,
    WriteRegW, WriteRegE,
    RegWriteM, MemtoRegM,
    WriteRegM,
    RegWriteE, MemtoRegE,
    rsE, rtE,
    rsD, rtD,
    jal,
    ForwardAE, ForwardBE,
    FlushE, StallID, StallIF, ForwardAD, ForwardBD, StallJal);

endmodule

module HazardUnit( input logic RegWriteW, BranchD,
    input logic [4:0] WriteRegW, WriteRegE,
    input logic RegWriteM, MemtoRegM,
    input logic [4:0] WriteRegM,
    input logic RegWriteE, MemtoRegE,
    input logic [4:0] rsE, rtE,
    input logic [4:0] rsD, rtD,
    input logic jalSignal,
    output logic [1:0] ForwardAE, ForwardBE,
    output logic FlushE, StallID, StallIF, ForwardAD, ForwardBD, output logic StallJal
    ); // Add or remove input-outputs if necessary

// *****
// Here, write equations for the Hazard Logic.
// If you have troubles, please study pages ~420-430 in your book.
// *****

logic lwstall;
logic branchstall;

always_comb

```

```

begin
    if ((rsE != 0 ) && (rsE == WriteRegM) && RegWriteM)
        ForwardAE = 2'b10;
    else if ((rsE != 0 ) && (rsE == WriteRegW) && RegWriteW)
        ForwardAE = 2'b01;
    else
        ForwardAE = 2'b00;

    if ((rtE != 0 ) && (rtE == WriteRegM) && RegWriteM)
        ForwardBE = 2'b10;
    else if ((rtE != 0 ) && (rtE == WriteRegW) && RegWriteW)
        ForwardBE = 2'b01;
    else
        ForwardBE = 2'b00;

    ForwardAD = (rsD != 0) && (rsD == WriteRegM) && RegWriteM;
    ForwardBD = (rtD != 0) && (rtD == WriteRegM) && RegWriteM;

    StallJal = jalSignal;

    lwstall = ((rsD == rtE) || (rtD == rtE)) && MemtoRegE;
    branchstall = (BranchD && RegWriteE && ( (WriteRegE == rsD) || (WriteRegE == rtD)) )
    || (BranchD && MemtoRegM && ( (WriteRegE == rsD) || (WriteRegE == rtD)));
    StallF = (lwstall || branchstall);
    StallD = (lwstall || branchstall);
    FlushE = (lwstall || branchstall);

end
endmodule

// You can add some more logic variables for testing purposes
// but you cannot remove existing variables as we need you to output
// these values on the waveform for grading
module top_mips (input logic clk, reset,
    output logic[31:0] instrF,
    output logic[31:0] PC, PCF,
    output logic PcSrcD,
    output logic MemWriteD, MemtoRegD, ALUSrcD, BranchD, jal,
    output logic [1:0] RegDstD,
    output logic RegWriteD,
    output logic [2:0] alucontrol,
    output logic [31:0] instrD,
    output logic [31:0] ALUOutE, WriteDataE,
    output logic [1:0] ForwardAE, ForwardBE,
    output logic ForwardAD, ForwardBD, output logic [31:0] jalAdressD, output logic
    StallJal, FlushE);

```

```

    controller CU(instrD[31:26], instrD[5:0], MemtoRegD, MemWriteD, ALUSrcD, RegDstD,
    RegWriteD, alucontrol, BranchD, jal);

```

```

    datapath DP(clk, reset, alucontrol, RegWriteD, MemtoRegD, MemWriteD, ALUSrcD,
    RegDstD, BranchD, jal,
        instrF, instrD,
        PC, PCF, PcSrcD,
        ALUOutE, WriteDataE,
        ForwardAE, ForwardBE, ForwardAD, ForwardBD, jalAdressD, StallJal, FlushE); // Add
    or remove input-outputs as necessary

```

```

endmodule

```

```

// External instruction memory used by MIPS
// processor. It models instruction memory as a stored-program
// ROM, with address as input, and instruction as output
// Modify it to test your own programs.

```

```

module imem ( input logic [5:0] addr, output logic [31:0] instr);

```

```

// imem is modeled as a lookup table, a stored-program byte-addressable ROM

```

```

    always_comb
        case ({addr,2'b00}) // word-aligned fetch

```

```

//

```

```

// *****

```

```

// Here, you can paste your own test cases that you prepared for the part 1-e.

```

```

// An example test program is given below.

```

```

// *****

```

```

//

```

```

//          address          instruction

```

```

//          -----          -

```

```

//      8'h00: instr = 32'h23FF0000; // add

```

```

//      8'h04: instr = 32'h23FF0000; // add

```

```

//      8'h08: instr = 32'h0c000000; // Jal 0

```

```

//      8'h10: instr = 32'h21080005;

```

```

//      default: instr = {32{1'bx}}; // unknown address

```

```

// Test code for no hazards

```

```

8'h00: instr = 32'h20080005; // addi $t0, $zero, 5

```

```

8'h04: instr = 32'h2009000c; // addi $t1, $zero, 12

```

```

8'h08: instr = 32'h200a0006; // addi $t2, $zero, 6

```

```

8'h0c: instr = 32'h210bff7; // addi $t3, $t0, -9

```

```

8'h10: instr = 32'h01288025; // or $s0, $t1, $t0

```

```

8'h14: instr = 32'h012a8824; // and $s1, $t1, $t2

```

```

8'h18: instr = 32'h010b9020; // add $s2, $t0, $t3
8'h1c: instr = 32'h010a202a; // slt $a0, $t0, $t2
8'h20: instr = 32'h02112820; // add $a1, $s0, $s1
8'h24: instr = 32'h02493022; // sub $a2, $s2, $t1
8'h28: instr = 32'had320074; // sw $s2, 0x74($t1)
8'h2c: instr = 32'h8c020080; // lw $v0, 0x80($zero)

// // Test code for Compute-use hazards
8'h30: instr = 32'h20080005; // addi $t0, $zero, 5
8'h34: instr = 32'h21090007; // addi $t1, $t0, 7
8'h38: instr = 32'h210A0002; // addi $t2, $t0, 2
8'h3c: instr = 32'h012A5025; // or $t2, $t1, $t2
8'h40: instr = 32'h01498024; // and $s0, $t2, $t1
8'h44: instr = 32'h01108820; // add $s1, $t0, $s0
8'h48: instr = 32'h0151902A; // slt $s2, $t2, $s1
8'h4c: instr = 32'h02318820; // add $s1, $s1, $s1
8'h50: instr = 32'h02329822; // sub $s3, $s1, $s2
8'h54: instr = 32'hAD330074; // sw $s3, 0x74($t1)
8'h58: instr = 32'h8C020080; // lw $v0, 0x80($zero)

// // Test code for load-use hazard
8'h5c: instr = 32'h20080005; // addi $t0, $zero, 5
8'h60: instr = 32'hac080060; // sw $t0, 0x60($zero)
8'h64: instr = 32'h8c090060; // lw $t1, 0x60($zero)
8'h68: instr = 32'h212a0004; // addi $t2, $t1, 4
8'h6c: instr = 32'h212b0003; // addi $t3, $t1, 3
8'h70: instr = 32'h8d6b0058; // lw $t3, 0x58($t3)
8'h74: instr = 32'h014b5022; // sub $t2, $t2, $t3
8'h78: instr = 32'hac0a0070; // sw $t2, 0x70($zero)
8'h7c: instr = 32'h8c080070; // lw $t0, 0x70($zero)
8'h80: instr = 32'h8d09006c; // lw $t1, 0x6c($t0)
8'h84: instr = 32'h01094820; // add $t1, $t0, $t1

// // Test code for branch hazard
8'h88: instr = 32'h20080005; // addi $t0, $zero, 5
8'h8c: instr = 32'h20090003; // addi $t1, $zero, 3
8'h90: instr = 32'h11090002; // beq $t0, $t1, 2
8'h94: instr = 32'h01285020; // add $t2, $t1, $t0
8'h98: instr = 32'h01094022; // sub $t0, $t0, $t1
8'h9c: instr = 32'h2129FFFF; // addi $t1, $t1, -1
8'ha0: instr = 32'h11280002; // beq $t1, $t0, 2
8'ha4: instr = 32'hac0a0050; // sw $t2, 0x50($zero)
8'ha8: instr = 32'h01284025; // or $t0, $t1, $t0
8'hac: instr = 32'h0128482A; // slt $t1, $t1, $t0
8'hb0: instr = 32'h11200002; // beq $t1, $zero, 2
8'hb4: instr = 32'h8c0b0050; // lw $t3, 0x50($zero)

```

```

8'hb8: instr = 32'h01284024; // and $t0, $t1, $t0
8'hbc: instr = 32'h1108FFFF; // beq $t0, $t0, -1

default: instr = {32{1'bx}}; // unknown address
endcase
endmodule

// *****
// Below are the modules that you should modify to add more instructions to the CPU
// *****

module controller(input logic[5:0] op, funct,
                  output logic memtoreg, memwrite,
                  output logic alusrc,
                  output logic [1:0] regdst,
                  output logic regwrite,
                  output logic[2:0] alucontrol,
                  output logic branch, jal);

    logic [1:0] aluop;

    maindec md (op, memtoreg, memwrite, branch, jal, alusrc, regdst, regwrite, aluop);

    aludec ad (funct, aluop, alucontrol);

endmodule

// External data memory used by MIPS single-cycle processor

module dmem (input logic clk, we,
             input logic[31:0] a, wd,
             output logic[31:0] rd);

    logic [31:0] RAM[63:0];

    assign rd = RAM[a[31:2]]; // word-aligned read (for lw)

    always_ff @(posedge clk)
        if (we)
            RAM[a[31:2]] <= wd; // word-aligned write (for sw)

endmodule

module maindec (input logic[5:0] op,
                output logic memtoreg, memwrite, branch, jal,
                output logic alusrc,
                output logic [1:0] regdst,

```

```

        output logic regwrite,
        output logic[1:0] aluop );
logic [9:0] controls;

assign {regwrite, regdst, alusrc, branch, jal, memwrite,
        memtoreg, aluop} = controls;

always_comb
case(op)
6'b000000: controls <= 10'b1010000010; // R-type
6'b100011: controls <= 10'b1001000100; // LW
6'b101011: controls <= 10'b0001001000; // SW
6'b000100: controls <= 10'b0000100001; // BEQ
6'b001000: controls <= 10'b1001000000; // ADDI
6'b000011: controls <= 10'b1100010000; // jal
default: controls <= 10'bxxxxxxxxxx; // illegal op
endcase
endmodule

module aludec (input logic[5:0] funct,
               input logic[1:0] aluop,
               output logic[2:0] alucontrol);
always_comb
case(aluop)
2'b00: alucontrol = 3'b010; // add (for lw/sw/addi)
2'b01: alucontrol = 3'b110; // sub (for beq)
default: case(funct) // R-TYPE instructions
6'b100000: alucontrol = 3'b010; // ADD
6'b100010: alucontrol = 3'b110; // SUB
6'b100100: alucontrol = 3'b000; // AND
6'b100101: alucontrol = 3'b001; // OR
6'b101010: alucontrol = 3'b111; // SLT
default: alucontrol = 3'bxxx; // ???
endcase
endcase
endmodule

module regfile (input logic clk, reset, we3,
               input logic[4:0] ra1, ra2, wa3,
               input logic[31:0] wd3,
               output logic[31:0] rd1, rd2);

logic [31:0] rf [31:0];

// three ported register file: read two ports combinationaly
// write third port on falling edge of clock. Register0 hardwired to 0.

always_ff @(negedge clk)

```



```

    if (reset)
        for (int i=0; i<32; i++) rf[i] = 32'b0;
    else if (we3)
        rf[wa3] <= wd3;

    assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
    assign rd2 = (ra2 != 0) ? rf[ra2] : 0;

endmodule

module alu(input logic [31:0] a, b,
           input logic [2:0] alucont,
           output logic [31:0] result,
           output logic zero);

    always_comb
        case(alucont)
            3'b010: result = a + b;
            3'b110: result = a - b;
            3'b000: result = a & b;
            3'b001: result = a | b;
            3'b111: result = (a < b) ? 1 : 0;
            default: result = {32{1'bx}};
        endcase

    assign zero = (result == 0) ? 1'b1 : 1'b0;

endmodule

module adder (input logic[31:0] a, b,
              output logic[31:0] y);

    assign y = a + b;
endmodule

module sl2 (input logic[31:0] a,
            output logic[31:0] y);

    assign y = {a[29:0], 2'b00}; // shifts left by 2
endmodule

module signext (input logic[15:0] a,
                output logic[31:0] y);

    assign y = {{16{a[15]}}, a}; // sign-extends 16-bit a
endmodule

// parameterized register

```

```

module flopr #(parameter WIDTH = 8)
    (input logic clk, reset,
     input logic[WIDTH-1:0] d,
     output logic[WIDTH-1:0] q);

    always_ff@(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= d;
endmodule

```

```

// paramaterized 2-to-1 MUX
module mux2 #(parameter WIDTH = 8)
    (input logic[WIDTH-1:0] d0, d1,
     input logic s,
     output logic[WIDTH-1:0] y);

```

```

    assign y = s ? d1 : d0;
endmodule

```

```

// paramaterized 4-to-1 MUX
module mux4 #(parameter WIDTH = 8)
    (input logic[WIDTH-1:0] d0, d1, d2, d3,
     input logic[1:0] s,
     output logic[WIDTH-1:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2 ) : (s[0] ? d1 : d0);
endmodule

```